

# LOOPHOLE

**FX TYPE: LOOPER**

©2011 madbeanpedals · Release date: 07.1.11

Traditionally, loopers have been a bit beyond the reach of analog DIY. While there are plenty of commercial digital (and probably some DIY designs) the choices for pedal hobbist with no programming experience have been limited. The **Loophole** is one project that attempts to bridge that gap. It is a low fidelity looper based off the ISD1020AP voice recorder chip. The ISD offers 20 sec. of digital recording at a sample rate of about 6.4kHz. All the A/D conversion is done within the chip, so designing an analog wrapper around it is a straight-forward task.

The Loophole originates from the Mobius Trip Looper designed by Dean Hazelwanter which has been available at General Guitar Gadgets for some time. Several modifications have been made to this design and features have been added to attempt to make this a more versatile project for all levels of DIY'ers. These include changes to the different gain stages in the analog path, noise reduction, a tone control for the loop and a hack that allows continuous detuning on playback.

It's important to know that this design cannot compete with commercially available digital loopers. It has significantly less fidelity and features than a Boss RC-3, for example. But, it does have its own character and definitely fits the mold of a worthy DIY build.

---

## **Controls**

**DRY:** Sets the dry signal volume of the guitar.

**VOL:** The overall output of the **DRY** and **PLAY** signal paths.

**PLAY:** Sets the volume of the playback loop.

**FILTER:** This is a "cut" type filter. Turning it clockwise reduces treble content.


**DTUNE:** This optional mod lets you apply continuous detuning to the playback via a momentary switch.

---

**This project requires a specific voice recorder IC.** The ISD1020AP is available from Smallbear, and it is the only source that I know of for purchasing. You may be able to find them on eBay, but this has not been researched.


ISD1020AP: <http://www.smallbearelec.com/Detail.bok?no=451>

## Layout Diagram

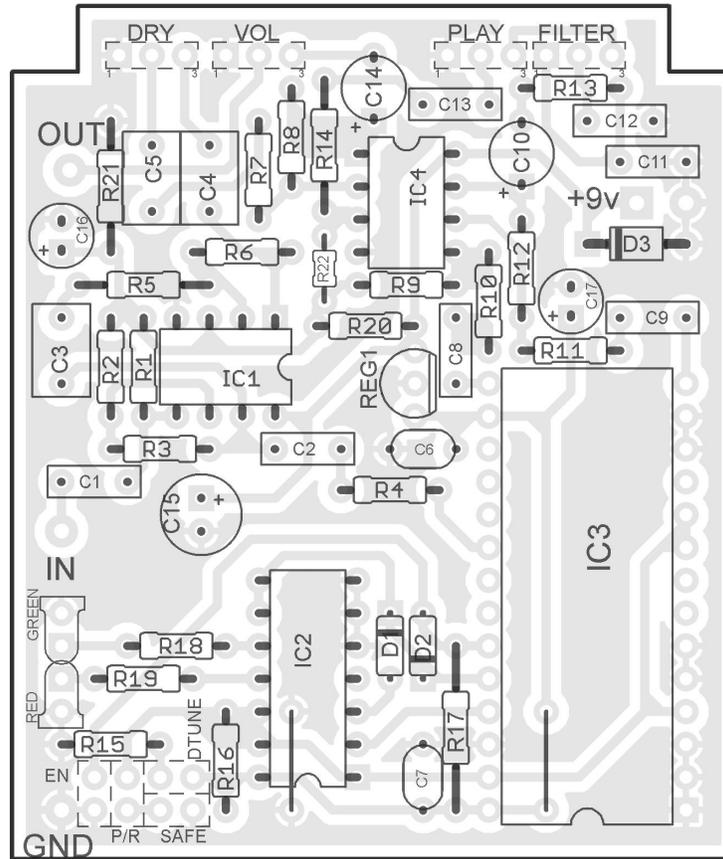


## Bill of Materials

Resistors		Caps		Diodes	
R1	470k	C1	100n	D1, D2	1n914
R2	10k	C2	100n	D3	1N4001
R3	10k	C3	100n	RED	LED
R4	10k	C4	100n	GREEN	LED
R5	10k	C5	100n	<b>IC</b>	
R6	22k	C6	100n	IC1	TL072
R7	10k	C7	100n	IC2	CD4001
R8	47k	C8	100n	IC3	ISD1020AP
R9	470k	C9	100n	IC4	TL072
R10	10k	C10	1uF	REG1	7805
R11	10k	C11	22n	<b>Switch</b>	
R12	22k	C12	220n	DTUNE	SPST
R13	1k	C13	100n	<b>Pots</b>	
R14	10k	C14	10uF	DRY	50k
R15	22R	C15	100uF	FILTER	10k
R16	47k	C16	10uF	PLAY	50k
R17	47k	C17	10uF	VOL	100k
R18	1k				
R19	1k				
R20	10k				
R21	10k				
R22	10k				

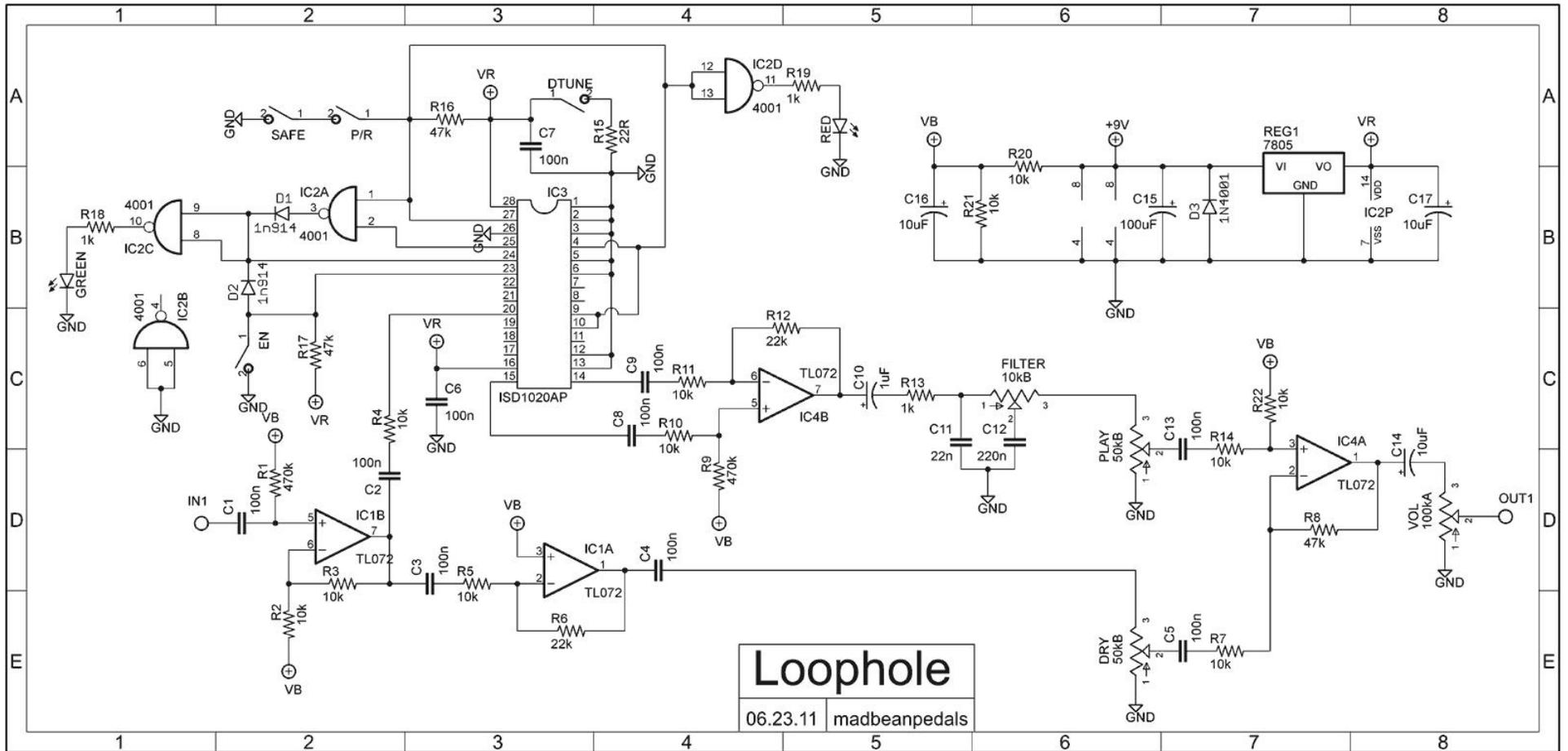
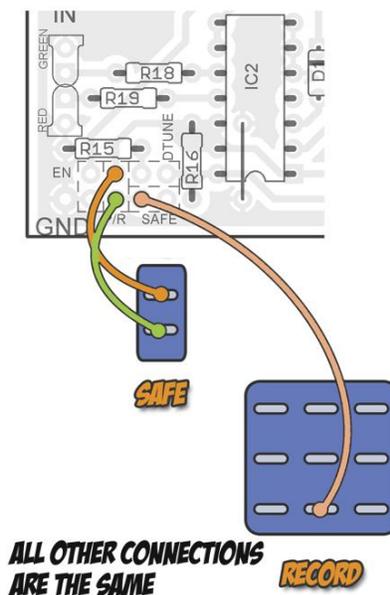
## Notes


- The **Loophole** is not true bypass. The input of the effect is always connected to the input jack, even when a loop is not recording. There are advantages and disadvantages to this approach. The biggest advantage is that looping can be done “on the fly” simply by toggling the **Record** switch without first having to disengage a bypass. The disadvantage is that there is a possibility of small signal loss. My own testing on the circuit seems to indicate that signal loss is at a minimum, and nothing on the level of say, an old Crybaby Wah.
- It is possible to make the **Loophole** true bypass by adding a third switch. This precludes any possible signal loss due to tone suckage. Note that if you do this, you will have to engage two switches to record a pass rather than one. Then toggle the **Record** switch off and the **Playback** switch on to enable the loop playback. This is a lot to remember and execute while actually playing your instrument. True bypass wiring has been omitted from this document.
- The **DETUNE** function allows continual playback detuning so long as the switch is engaged. You can use either a latching or momentary switch. The small switch pictured in the build below (between the two 3PDTs) was purchased from Tayda Electronics and is a momentary. If you plan on using a larger enclosure, such as a 1590BB, a momentary footswitch would be a great addition. Note that you can also apply the **DETUNE** when recording a loop. When playing a de-tuned loop in playback, the pitch will increase continuously. This momentary footswitch is about the same size as a 3PDT and will work well for foot control: <http://www.smallbearelec.com/Detail.bok?no=672>
- Pads are included for a “Safe” switch on the PCB. The Safe switch disables recording by the voice recorder chip and will prevent accidental erasing of a loop you wish to save. Note that the **Loophole** will store any recorded loop until it is over-written, even when the power is disconnected. The Safe switch adds one more layer of protection by making it impossible to record anything into the chip. To add a Safe switch, refer to the following diagram:



- You can experiment with adding an effects loop to the Loophole with a simple modification. R4 sets the record level into the ISD chip. Remove this resistor and use the two free pads for a send and return. By doing this, the **Loophole** will record the effected signal into the looper, and the output of the inserted effect sets the record level. Note that this has not been verified.
- This type of DC jack has a smaller profile and is a snap-in rather than using a nut. I recommend this if you are building the **Loophole** into a 1550B or 1590B. It does not have a ring for battery operation, but will allow you to place the jack very close to the top of the enclosure. See the pictures at the end of this document to get an idea.  
<http://www.mouser.com/ProductDetail/163-1000-EX/?qs=sGAEpiMZZMtiLeikjuthVh%2f8HnDmxZQr>


## HOW TO RECORD AND PLAY A LOOP

### STEP 1

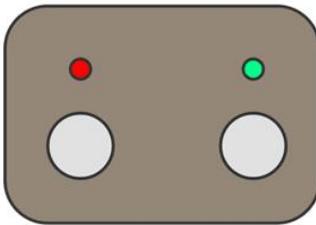


BOTH THE RECORD AND PLAYBACK SWITCHES ARE OFF. THIS IS THE (NON TRUE) BYPASS MODE.

### STEP 2

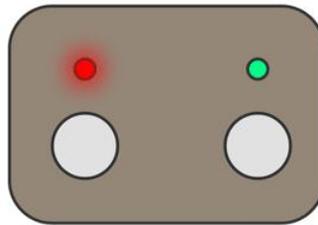


TOGGLE THE LEFT SWITCH TO ENABLE RECORDING. BEGIN PLAYING THE PHRASE TO BE LOOPED AT THE SAME TIME.


### STEP 3

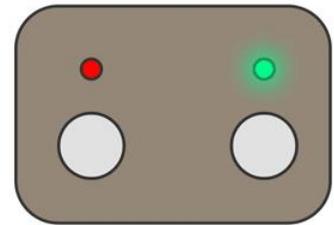


ONCE THE PHRASE HAS BEEN PLAYED, TOGGLE THE LEFT SWITCH AGAIN TO STOP RECORDING. NOW TOGGLE THE RIGHT SWITCH TO PLAY THE LOOP BACK.

2.21"W x 2.61"H

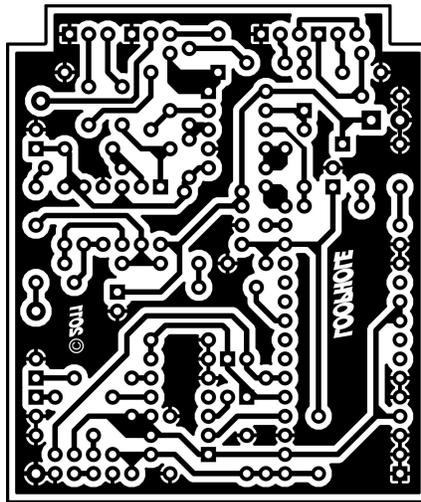

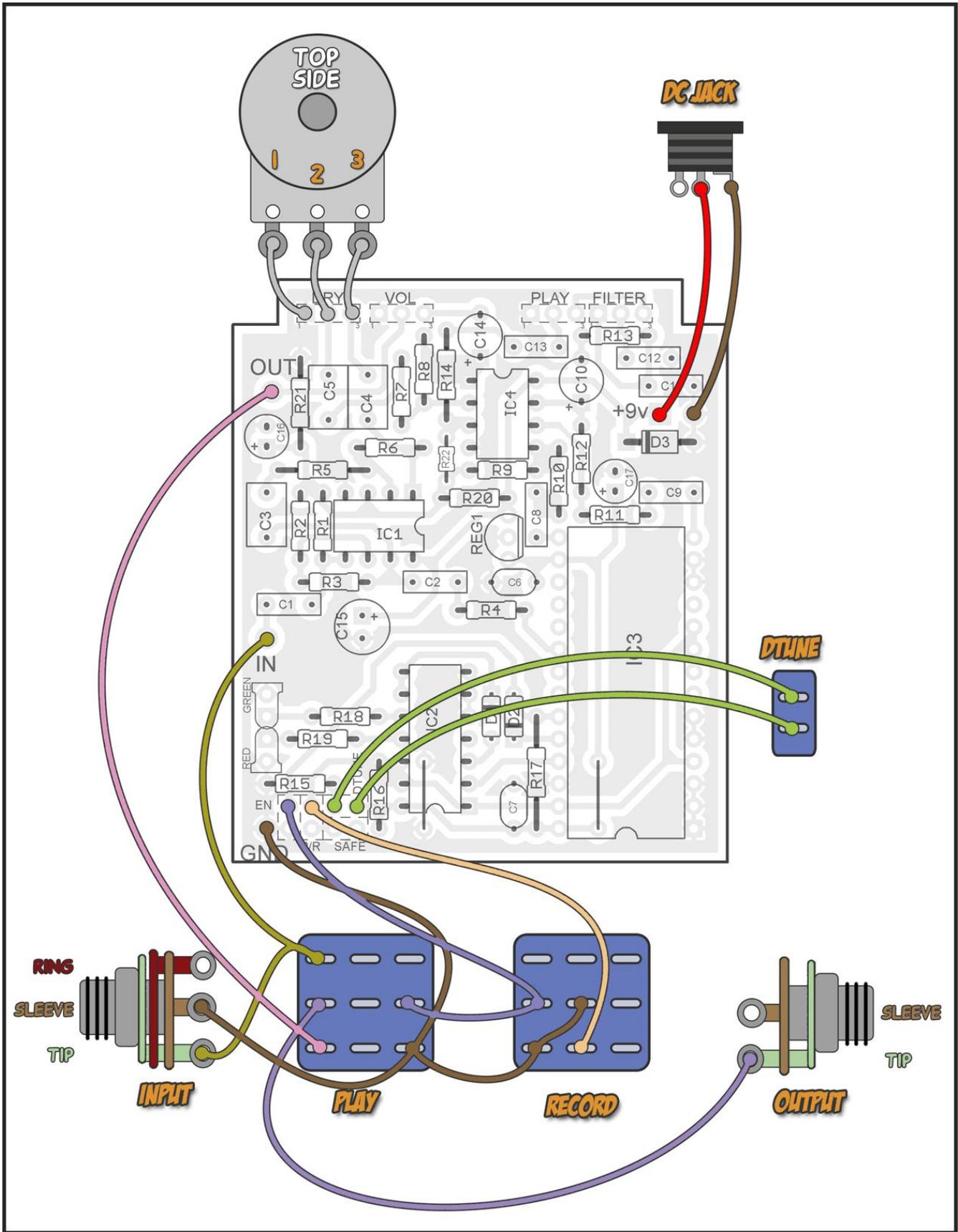

**4.33" x 6.3"**  
**1550B**

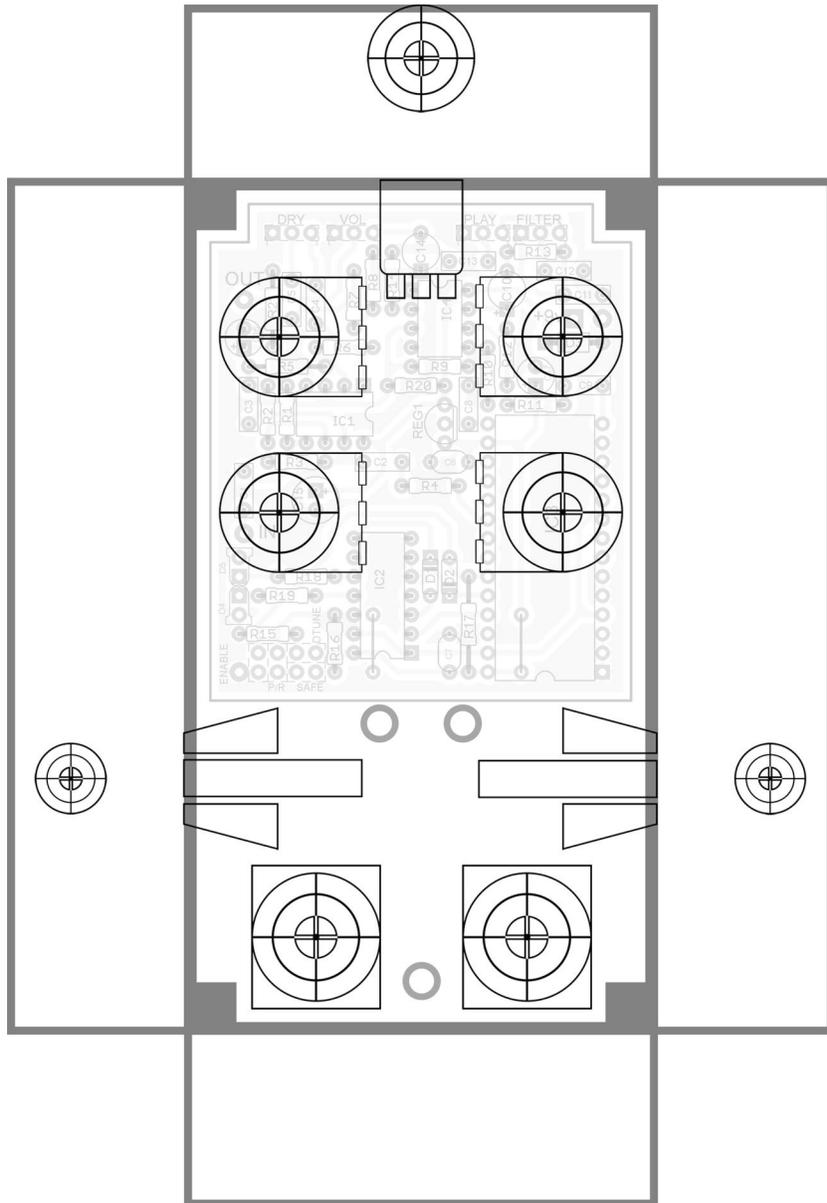

The Hammond 1550B is slightly wider and longer than the 1590B and is what I used for my build. I highly recommend this enclosure over the 1590B if you want to do a two switch layout.

The 1550 can be ordered from Mouser in either black powder coated or unfinished.

<http://www.mouser.com/Search/Refine.aspx?Keyword=hammond+1550b>



## Terms of Use



The madbeanpedals effects projects and PCB products are available for non-commercial use to all DIY enthusiasts, hobby builders and pedal makers. They are not intended, nor should they be used, for commercial manufacturing. This means that the PCBs and information in the project documents should not be utilized in the context of professional pedal making. However, building the projects for yourself or your friends or making the occasional “one-off” for sale is entirely permissible. The sale of PCBs or kits using the included PCB artwork is strictly prohibited, however.

Please keep in mind that some of the madbeanpedals projects are based upon currently manufactured pedals. Using the projects or PCBs to make cheap knock-off pedal clones for sale on eBay is not only not cool, but potentially hazardous to your karma. While the vast majority of guitar effects circuits are not patented, many pedal manufacturers do hold trademarks over their products. Any attempt to infringe on a manufacturer’s trademark could be met with legal challenges, and madbeanpedals offers no warranty or guarantee against this, should you do so.

**build.share.learn.**